

CHIPAssignment Project Examile USE

https://eduassistpro.github.io/

Add WeChat edu_assist_pro

Bernhard Kainz (with thanks to

N. Dulay and E.

Edwards)

b.kainz@imperial.ac.uk

Integrated Circuits

All ICs (chips) are made up of logic gates

ICs are squares interest Bilingos to Example by the logic gates have been depo https://eduassistpro.github.io/

Generally rows of dish Weralbet edu_assistorptooa larger circuit



Assignment Project Exam Help

https://eduassistpro.github.io/

IC – Sizes

NameAssignme	nt Project Exam	Help Number of Gates
Small Scale Integra	//aduaccietara	withub io ¹⁻¹⁰
Medium Scale Integr	// Cuuassistpi o. ţ	10-100
Large Scale Integrated V	WeChat edu_as	sist_ ppo -100,000
Very Large Scale Integrated	VLSI	>100,000

Example SSI Chips

Assignment Project Exam Help

https://eduassistpro.github.io/

Add WeChat edu_assist_pro

7404 – hex inverter

Example Circuit with SSI/MSI Chips

Assignment Project Exam Help

https://eduassistpro.github.io/

- A multiple-input, single-output switch
- Also called MUX for short ©

Assignment Project Exam Help

https://eduassistpro.github.io/

- sel selects which of I₀ or I₁ is mapped to the output
- For example, sel = 0 selects I_0 and sel = 1 selects I_1
- Example is called a 2-to-1 MUX
- With n selects/control lines, we can have 2ⁿ input lines

2-to-1 Multiplexer

Assignment Project Exam Help

https://eduassistpro.github.io/

Add WeChat edu_assist_pro

Source: http://www.sparkfun.com/tutorials/371

Truth Table

A A	ssi g nm	entxPro	jest Ex	ar n H el	рү
0	•			0	0
0	https	s://edua	issistpr	o.g _l thu	D.IQ/
0	Ådd	WeCh	at edu	assist	pro
0	1	1	at Gaa_	<u> </u>) 1
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	0	1	1

• The 3 inputs **A**, **B**, **C**select which of the
Assignment Project Example (D₀-D₇) is
https://eduassistpro.githrough to the
Add WeChat edu_assist_pro

 In general, a multiplexer has 2ⁿ inputs and n control lines and one output

• Fits nicely into a 14-pin package (with ground Assignment Project Franklelp

https://eduassistpro.github.io/

- A single-input, multiple-output switch
 - Opposite of a MUX
- · Also called A Ment Project Exam Help
- Usually used in

https://eduassistpro.github.io/

MSI Chips – Decoder

- A multiple-input, multiple-output logic circuit
 - · Converts coded ignitainte project textam Help
 - Binary Decoder https://eduassistpro.github.io/
 - Necessary in applied on sechat edu_assisting and memory address decoding

MSI Chips – Decoder

Only one output is 1 – the Assignment Project Feetber by the n-bit put number – the https://eduassistpro.github.io/

Add WeChat edu_assist_pro

ransmitting line selection with fewer wires (e.g. selecting a memory chip)

MSI Chips – Decoder

Truth Table

Α	BA	ssig	nPae	rR ₆ F	reie	cP4E	ixan	n H e	18	D_0
0	0	0			7			0	0	1
0	0	1h	ttps	://ec	luas	sist	pro.	gith	ub.id	0/0
0	1	0	0	0	0	ا م		-:-4	0	0
0	1	1 A	agi	We(_nai	eat	ı_as	sist	-Bro	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

MSI Chips – Calculations – Comparator

- To compare two numbers
- Example: 1-bit comparison
 - · Which gate Assignment Project Exam Help
 - Recall: https://eduassistpro.github.io/

A	Agd	Wech	at edu_assist_pro
0	0	0	
0	1	1	
1	0	1	
1	1	0	

MSI Chips – Calculations – Comparator

Assignment Project Exam Help

https://eduassistpro.github.io/ parator r 1 Add WeChat edu_assistbip roputs A and I, 0 otherwise

MSI Chips – Calculations – Bit-shifter

- Faster calculations for powers of 2
- Shift left and right (multiply and divide)
 Assignment Project Exam Help

https://eduassistpro.github.io/

- $c = 0 \rightarrow \text{shift left}$
- $c = 1 \rightarrow \text{shift right}$

The Arithmetic Logic Unit (ALU)

- Digital circuit that performs arithmetic and logical operations
- Fundamental building block of the central processing unit (CPU) of a computer
 - Even the simplest maintaining timer https://eduassistpro.github.io/
 - Processors found inside modern CP ics processing units (GPUs) accommodated by powerfuedu_assistplexQLUs
- Concept proposed in 1945 by Mathematician John von Neumann
- Research into ALUs remains an important part of computer science

ALU

Recall: Full Adder

Assignment Project Exam Help

https://eduassistpro.github.io/

The Arithmetic Logic Unit (ALU)

Assignment Project Exam Attelp able to perform iple functions https://eduassistpro.github.io/

Add WeChat edu_assisted Property, property one of four functions is selected — A and B, A or B, not B,

arithmetic A+B

8-bit ALU

- Can link together 1-bit ALUs to form a multi-bit ALU
 - Sometimes known as bit-slice circuits

Assignment Project Exam Help

https://eduassistpro.github.io/

CPU Design – VLSI

Contains millions of gates – same structure as below

Assignment Project Exam Help

https://eduassistpro.github.io/

CPU Design – VLSI

Assignment Project Exam Help

https://eduassistpro.github.io/

Production

- Good video: https://www.youtube.com/watch?v=vK-geBYygXo
- Bad video: Assignment Project Exam Help https://www.you aQJSyP8 https://eduassistpro.github.io/